



Figure 1: A simple circuit illustrating how a motor, with resistance, R_{motor} , will generate a “back emf”, equivalent to a battery that produces a voltage in the direction to oppose the current from the actual battery that is powering the motor, ΔV .